

Objectives:


The objective for this week will be to do detailed discussion on universal gates, their possible uses along with practice examples. Basically, in these lectures, I will teach you to design all the gates with the help of universal gates (nand, nor). So, in case, you are left with only universal gates, you can design all other gates with the help of these gates without buying new gates.

- NAND Implementation
- NOR Implementation
- PLD
- Function Implementation on PROM


LECTURE-21

NAND IMPLEMENTATION

NOT GATE

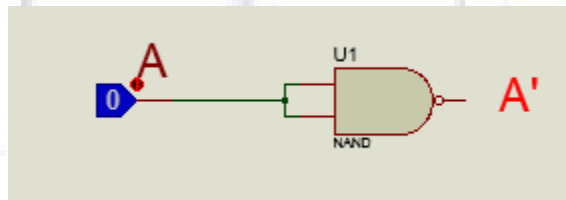

AND GATE

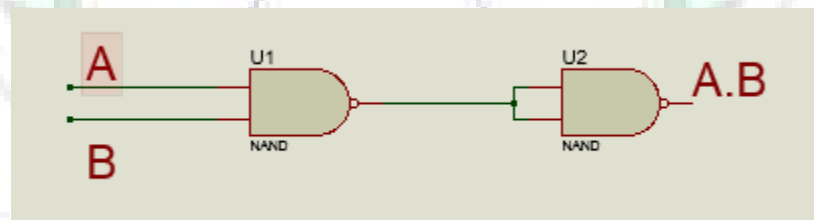


OR GATE

Digital Logic Design (ESC-151)


Abdul Rehman

email id:- abdul@northern.edu.pk


Whatsapp#03087792217

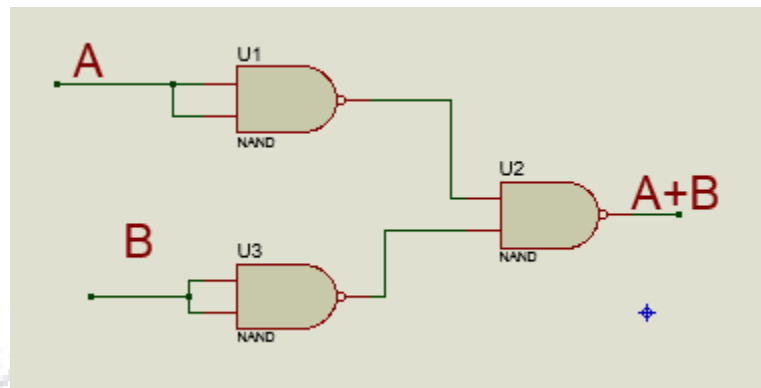

NOR GATE

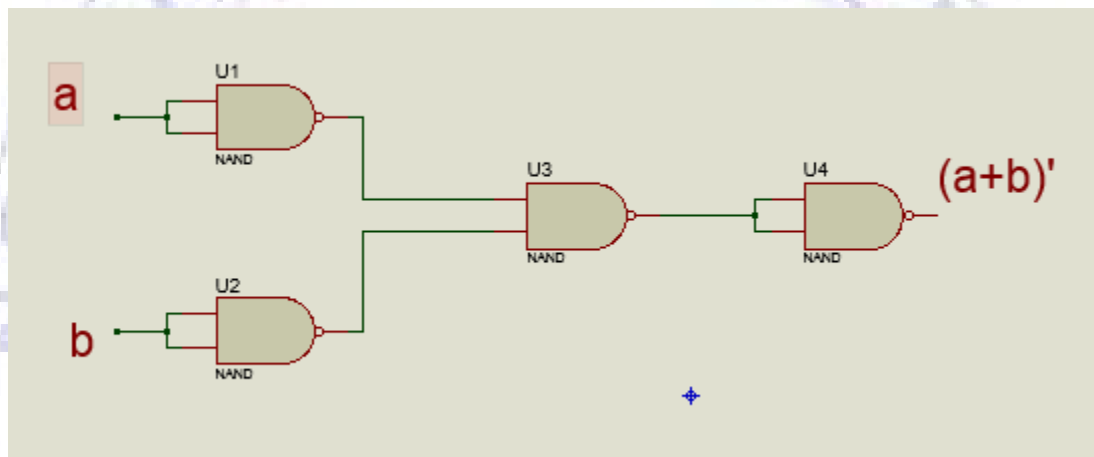

NAND GATE

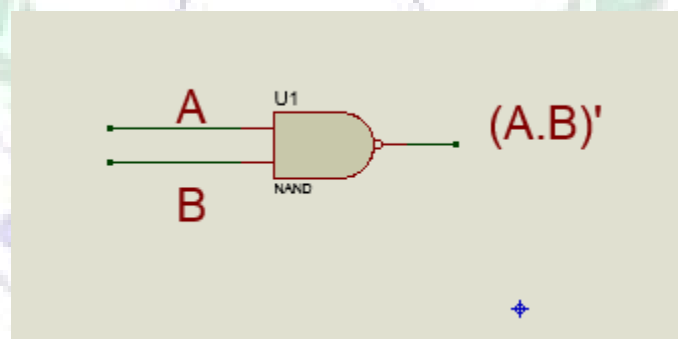


XOR GATE (A'B+AB')

Digital Logic Design (ESC-151)


Abdul Rehman

email id:- abdul@northern.edu.pk

Whatsapp#03087792217

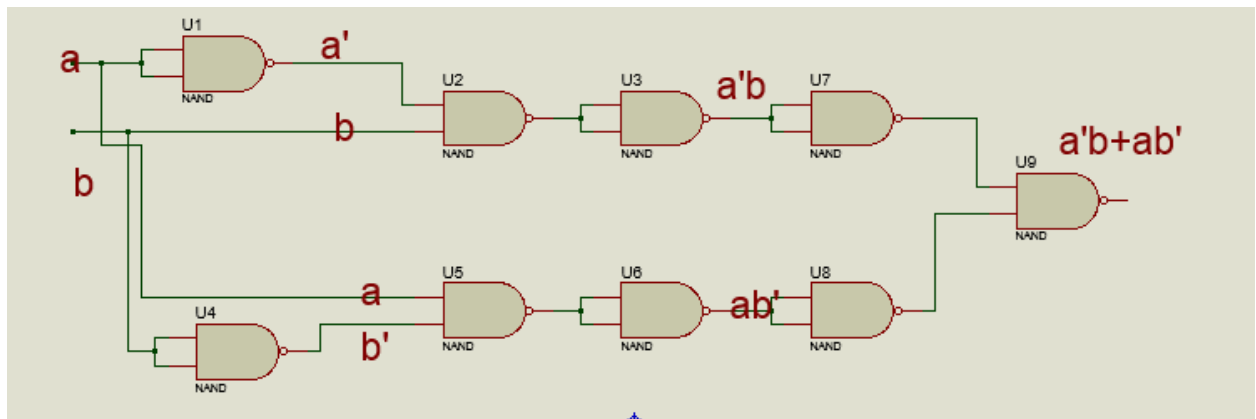

XNOR GATE

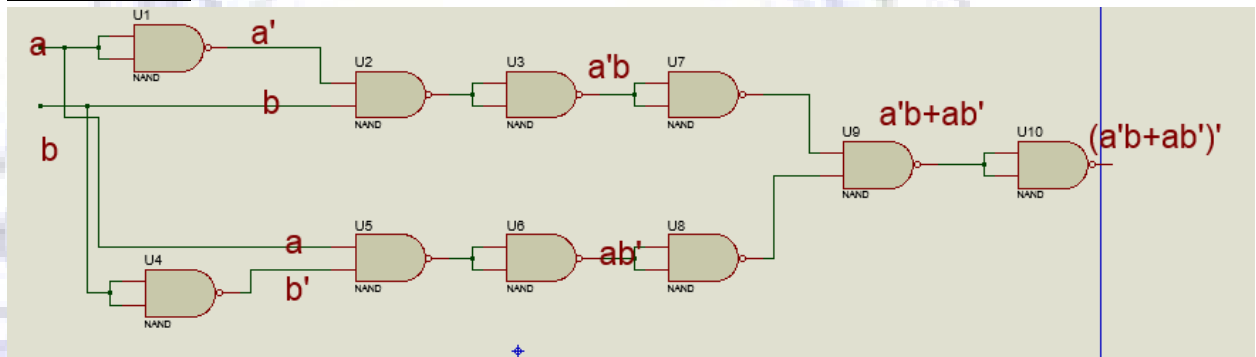

:PRACTICE EXAMPLES:

Scenario#1

Equation To Circuit:


$$\{(A+B')C\}' + (BC)'$$

Digital Logic Design (ESC-151)

Abdul Rehman


email id:- abdul@northern.edu.pk

Whatsapp#03087792217

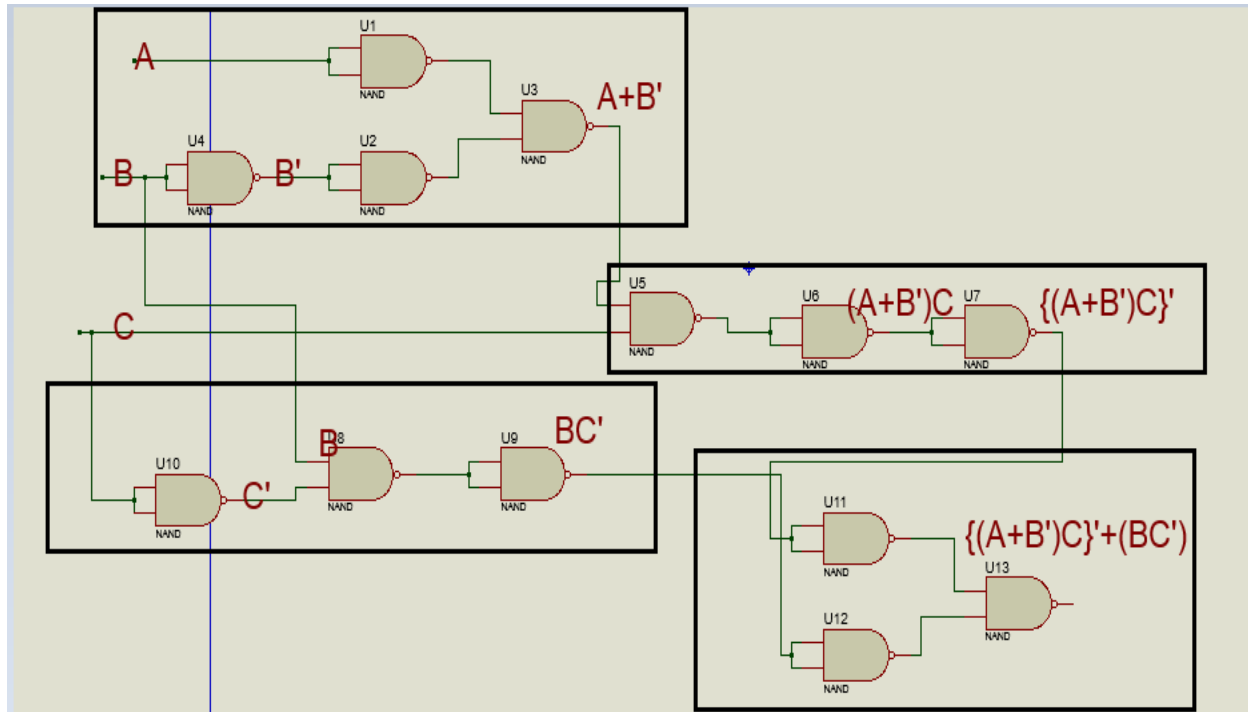

Scenario#2

Block Diagram To Circuit:

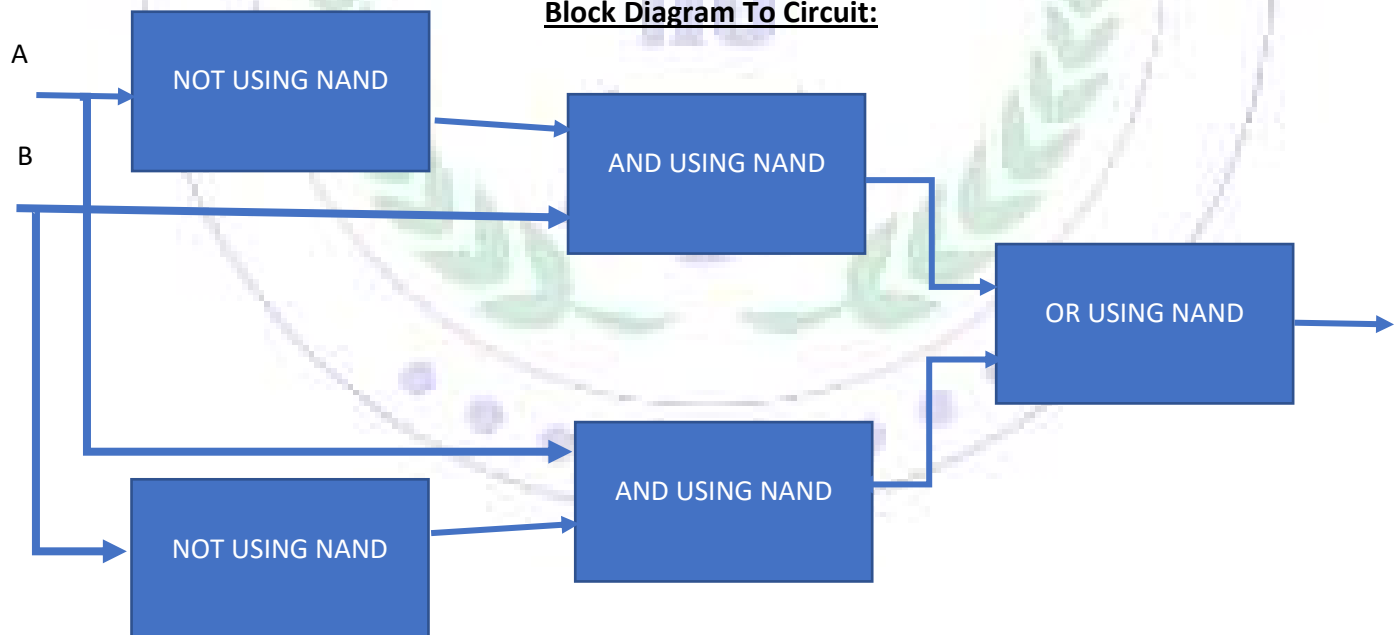


Digital Logic Design (ESC-151)

Abdul Rehman


email id:- abdul@northern.edu.pk

Whatsapp#03087792217

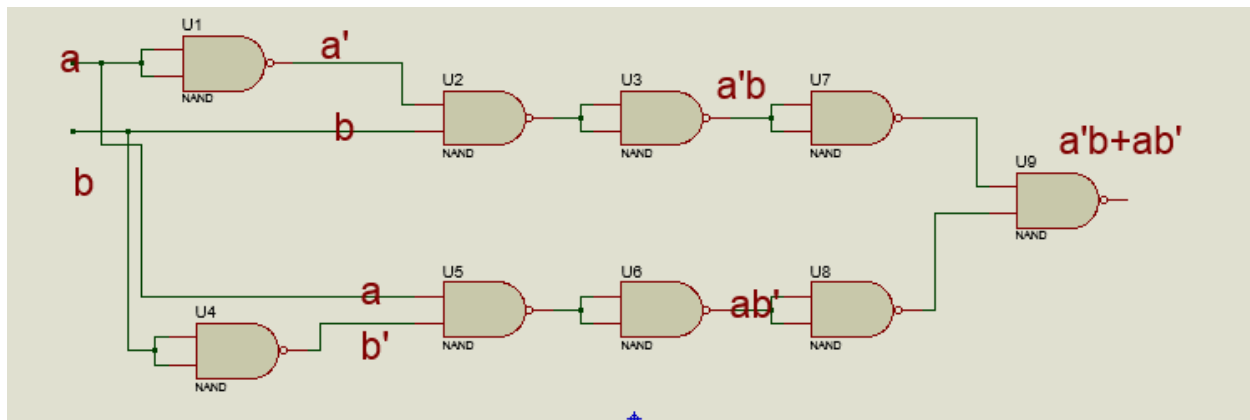

Scenario#3

Circuit To Circuit Conversion:

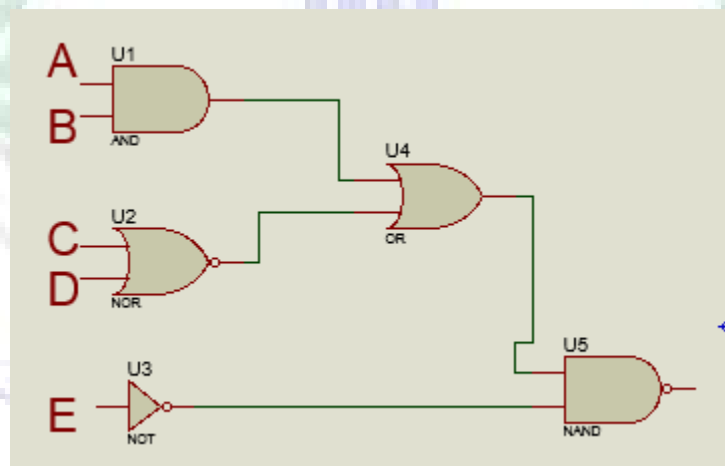


Solution:

Digital Logic Design (ESC-151)

Abdul Rehman


email id:- abdul@northern.edu.pk

Whatsapp#03087792217

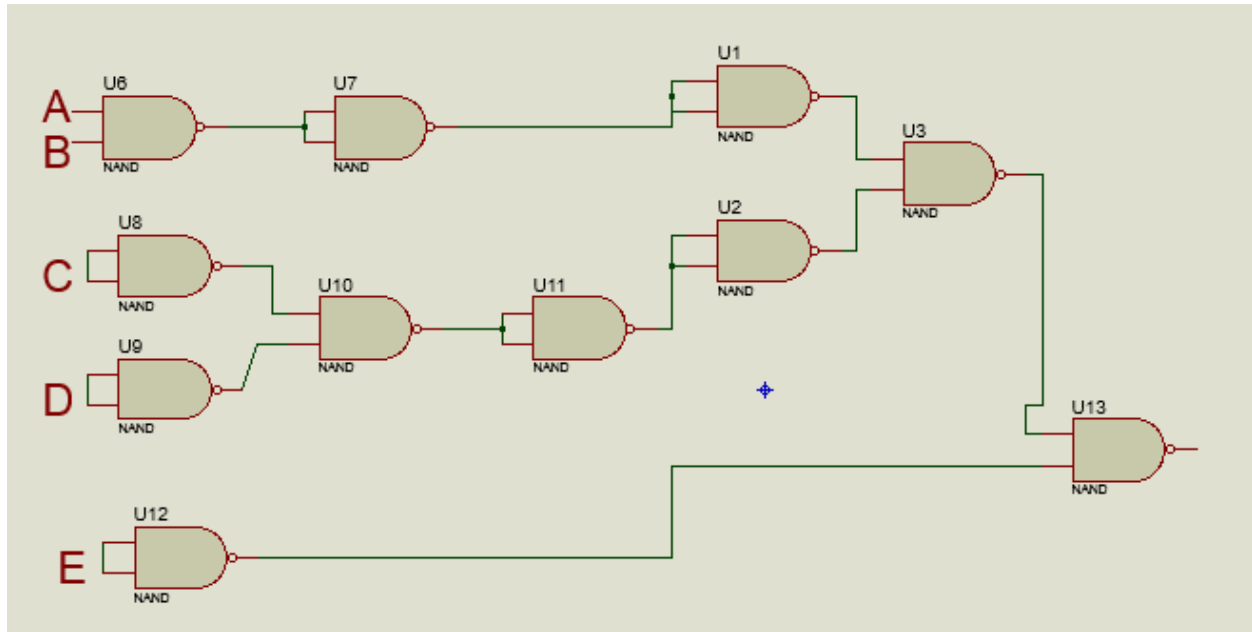


NOR Implementation

NOT GATE

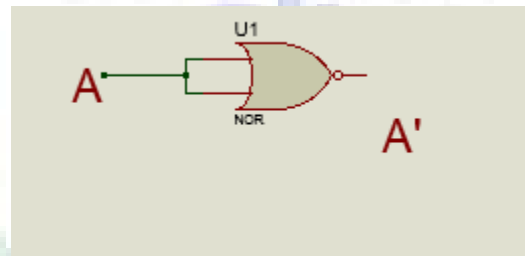

OR GATE

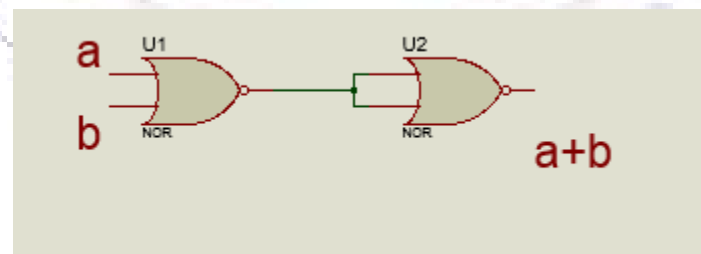


AND GATE

Digital Logic Design (ESC-151)


Abdul Rehman

email id:- abdul@northern.edu.pk


Whatsapp#03087792217

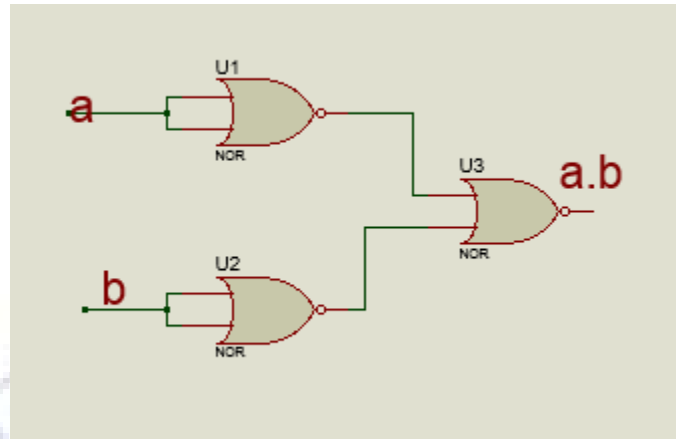

NOR GATE

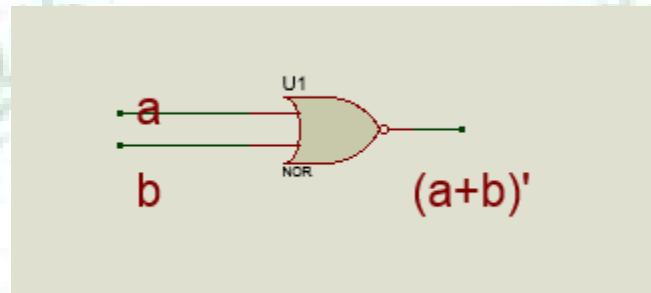

NAND GATE

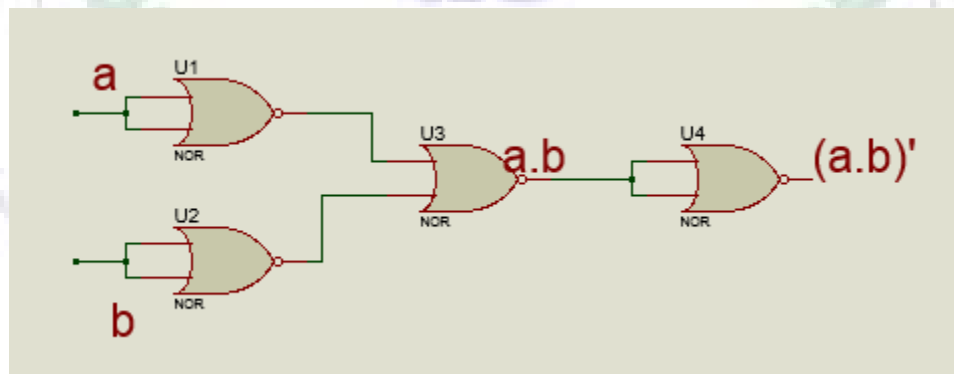


XOR GATE

Digital Logic Design (ESC-151)


Abdul Rehman

email id:- abdul@northern.edu.pk

Whatsapp#03087792217

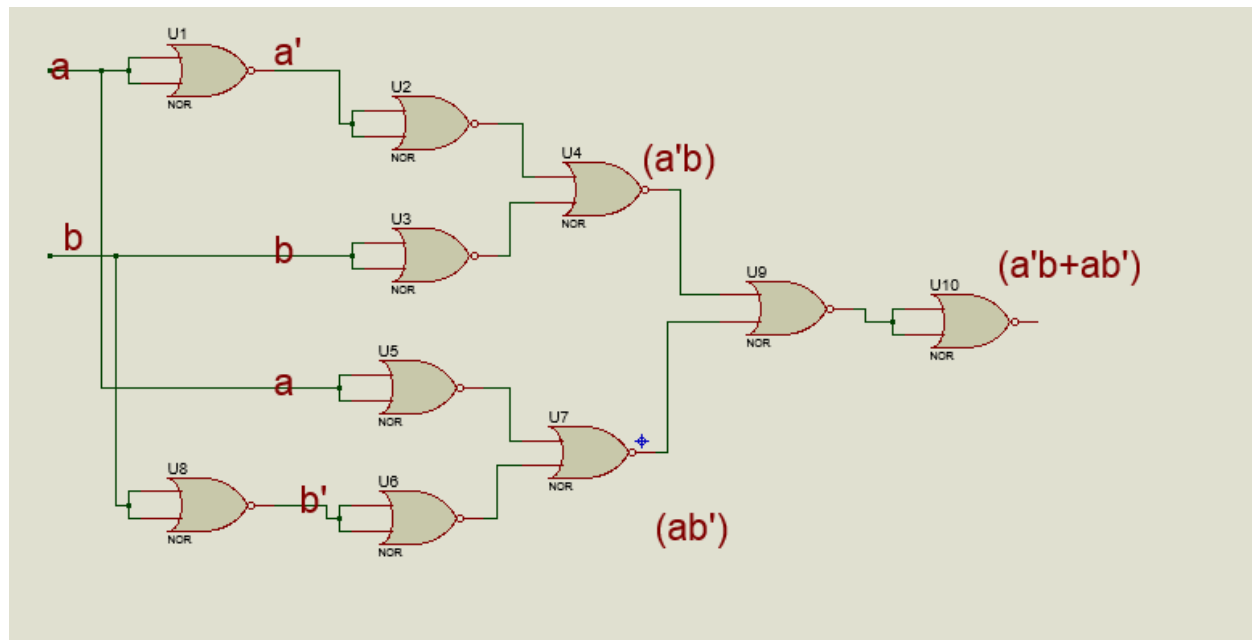

XNOR GATE

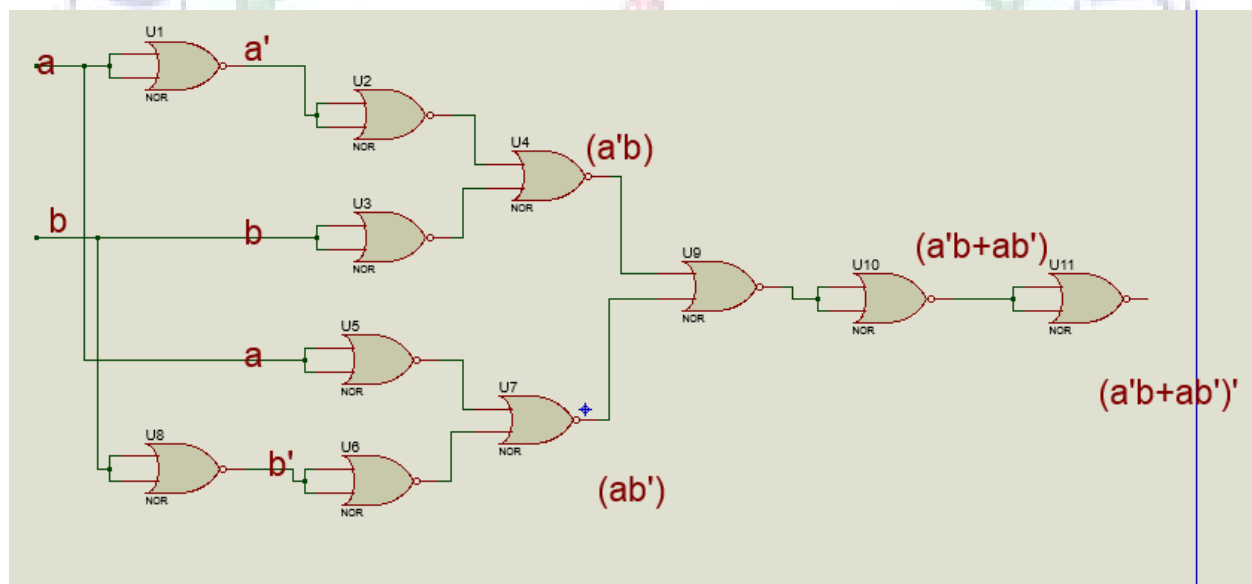

:Practice Examples:

Scenario#1:

Digital Logic Design (ESC-151)

Abdul Rehman


email id:- abdul@northern.edu.pk

Whatsapp#03087792217

Equations To Circuit:

$$(AB'C+AC')'+(BXORC)$$

General Circuit Before Conversion:

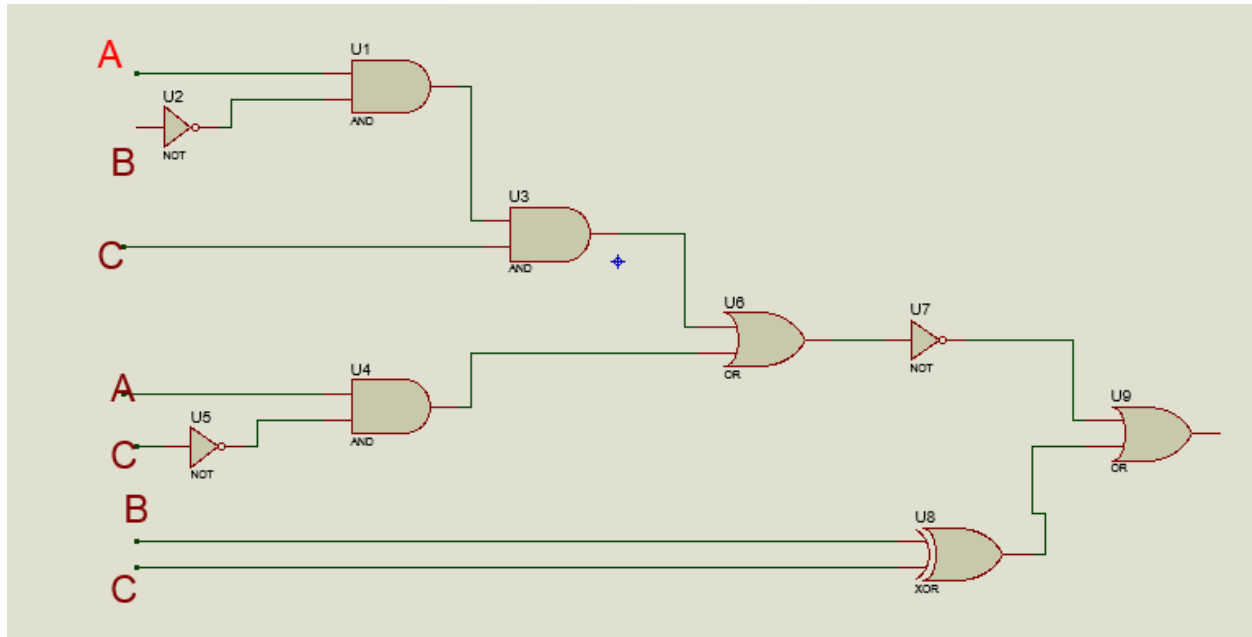

After Conversion, Final Circuit Diagram:




Digital Logic Design (ESC-151)

Abdul Rehman


email id:- abdul@northern.edu.pk

Whatsapp#03087792217

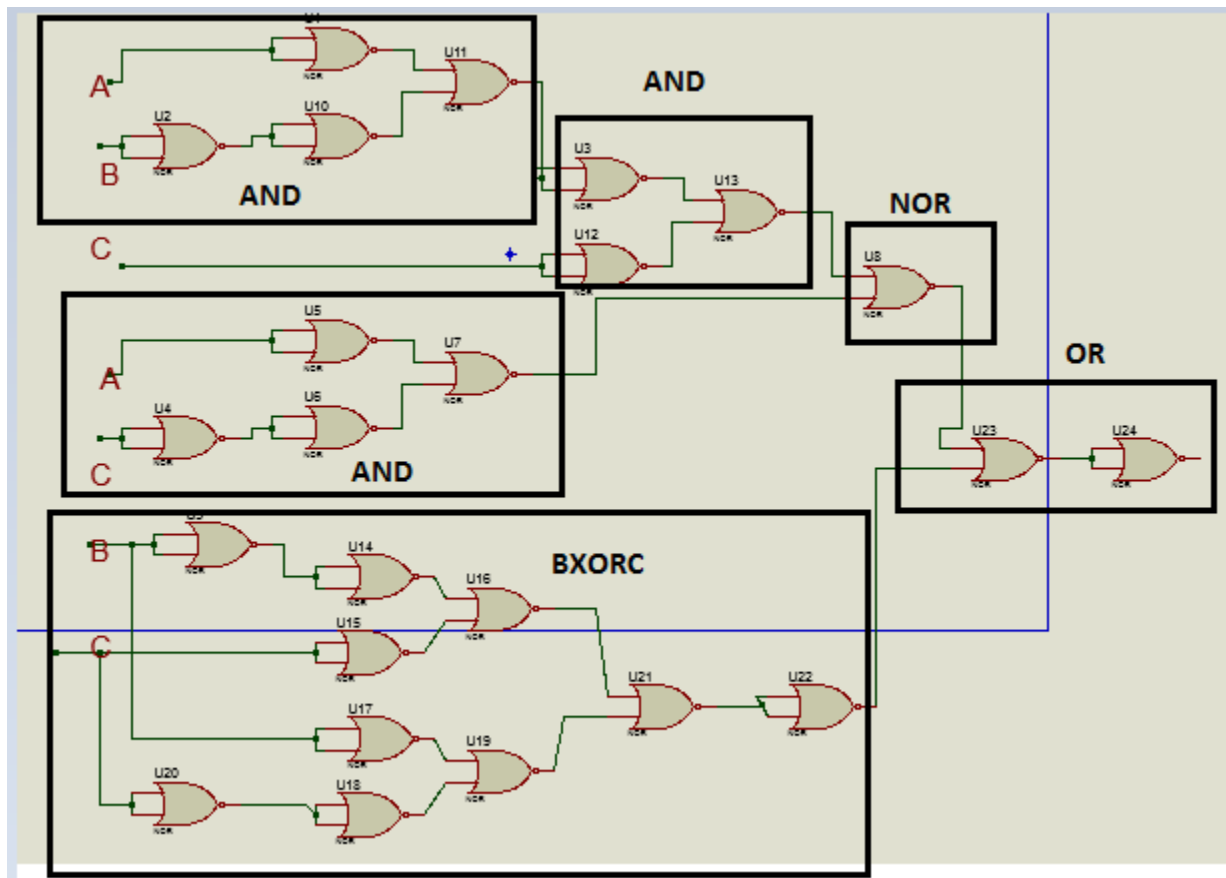

Scenario#2

Block Diagram To Circuit:

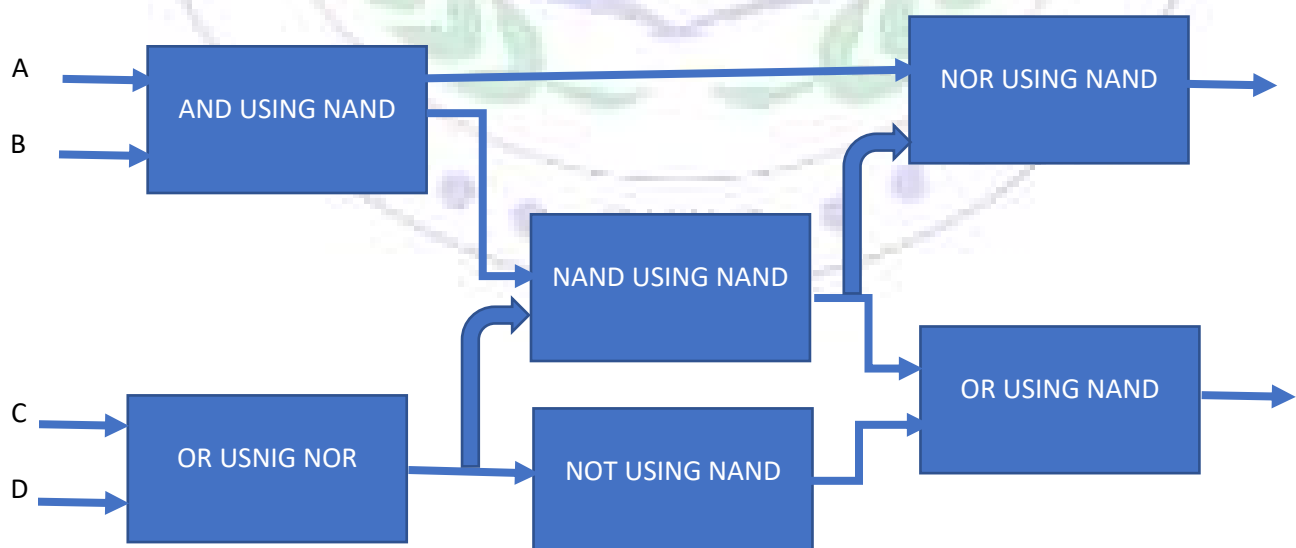


Digital Logic Design (ESC-151)

Abdul Rehman


email id:- abdul@northern.edu.pk

Whatsapp#03087792217

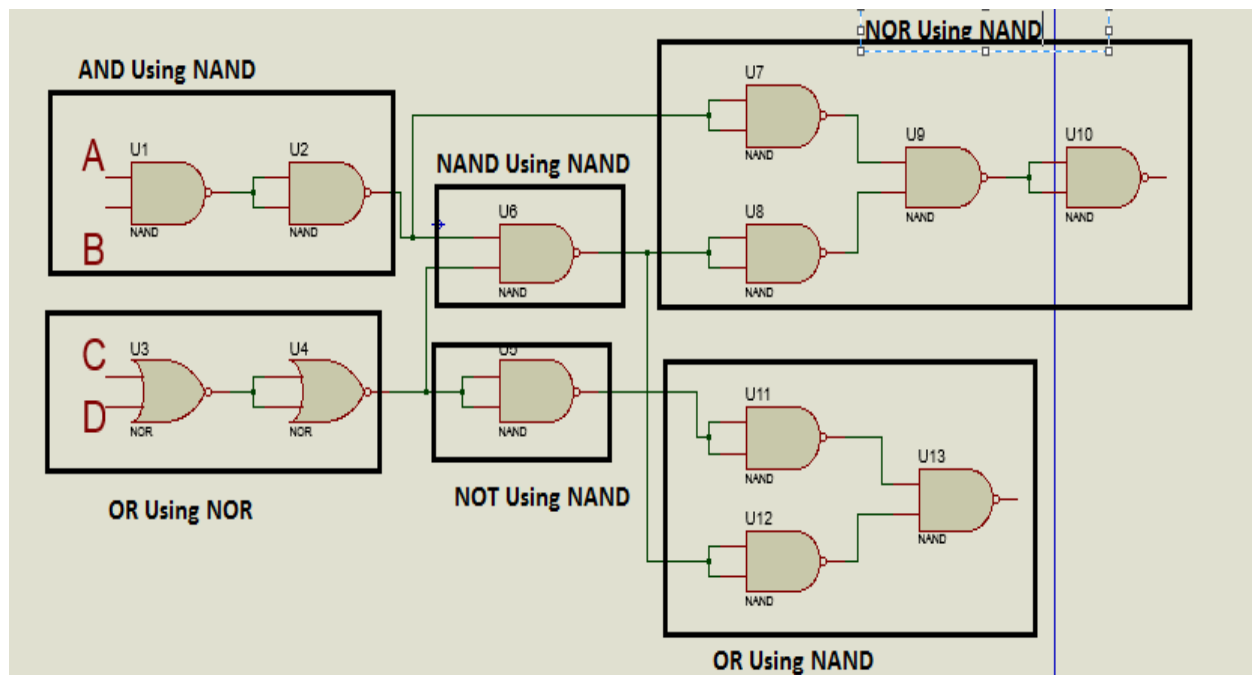

Scenario#3

Circuit To Circuit Conversion:

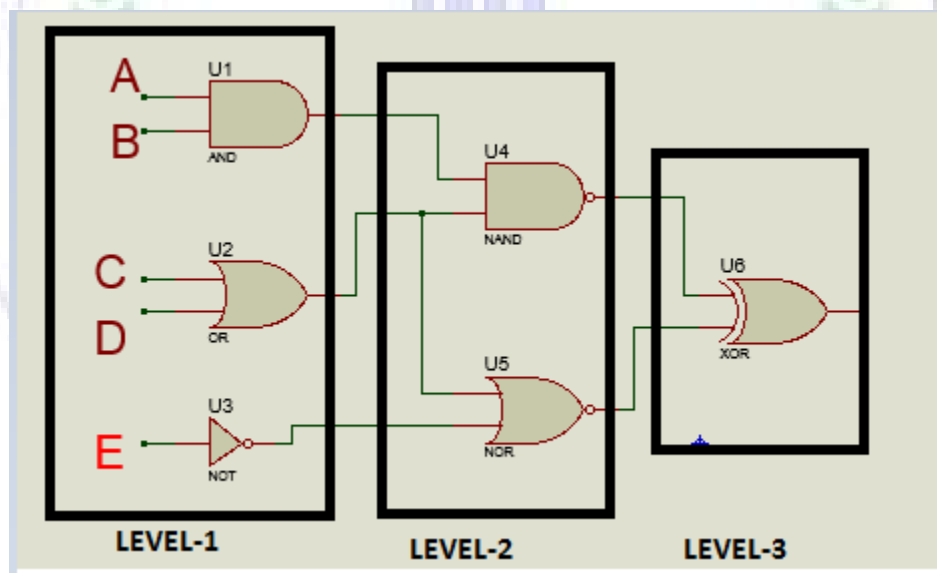

- Solve Level-1 Using Equivalent NAND Implementation
- Solve Level-2 Using Equivalent NOR Implementation
- Solve Level-3 Using Equivalent NAND Implementation


Solution:

Digital Logic Design (ESC-151)


Abdul Rehman

email id:- abdul@northern.edu.pk

Whatsapp#03087792217

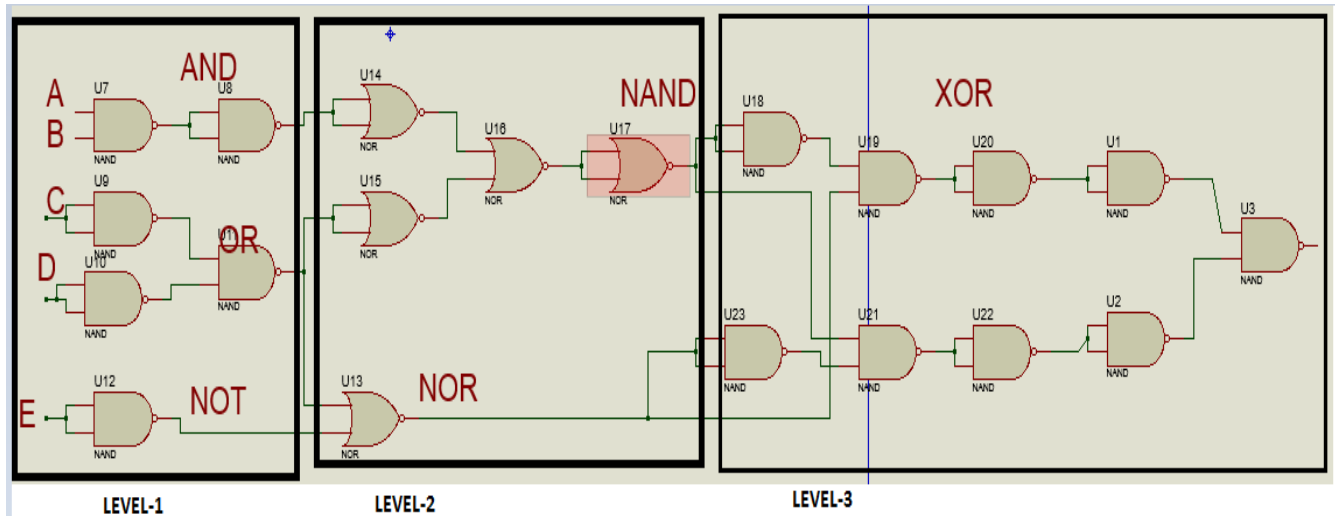

LECTURE-22

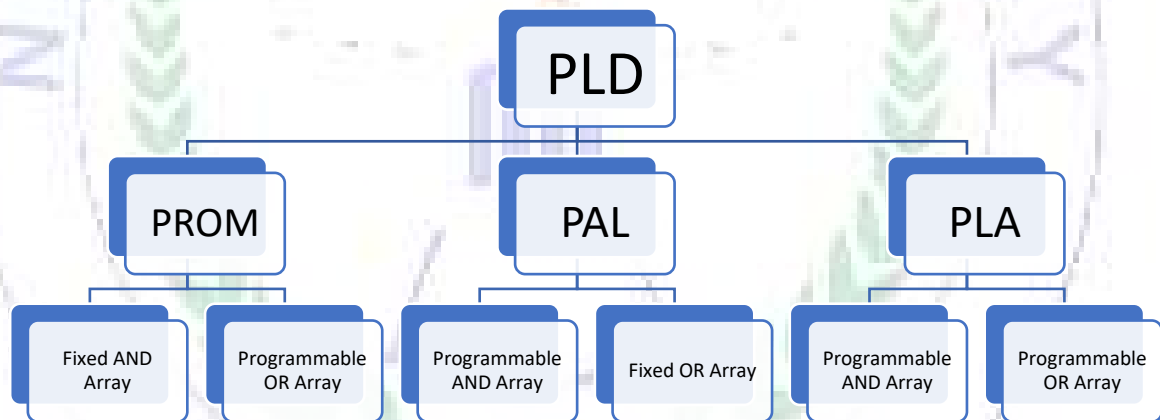

Important Points:


- Combination of AND-OR Array
- Hardware level Programming
- Fuses are used
- NOT gate can be used
- Symbols:

Digital Logic Design (ESC-151)

Abdul Rehman

email id:- abdul@northern.edu.pk

Whatsapp#03087792217

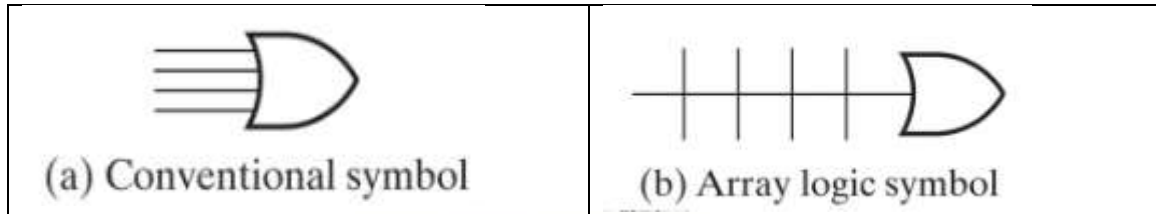

ROM Types:

1. ROM (Masking)
2. PROM (Programmable ROM)
3. EPROM (Erasable PROM)
4. EEPROM/ E²PROM (Electrically Erasable PROM)

PROM Programming:

- Fixed AND Array
- Programmable OR Array

Note:

- ✓ For AND Array, decoder will be used. (to decide the order of the decoder, see the input variables of given function to be embedded on the ROM)
- ✓ For OR Array, OR gates will be used. (to decide number of OR gates to be used, see the number of functions given)

Lets get started:

Example#1:

Design following output functions on an 8x2 PROM:

<u>A</u>	<u>B</u>	<u>C</u>	<u>F₁</u>	<u>F₂</u>
0	0	0	1	0
0	0	1	1	1
0	1	0	1	0
0	1	1	0	0
1	0	0	0	1
1	0	1	1	0
1	1	0	0	1
1	1	1	1	0

Digital Logic Design (ESC-151)

Abdul Rehman

email id:- abdul@northern.edu.pk

Whatsapp#03087792217


$$F_1 = A'B'C' + A'B'C + A'BC' + AB'C + ABC$$

$$F_2 = A'B'C + AB'C' + ABC'$$

OR

$$F_1 = \sum(m_0, m_1, m_2, m_5, m_7)$$

$$F_2 = \sum(m_1, m_4, m_6)$$

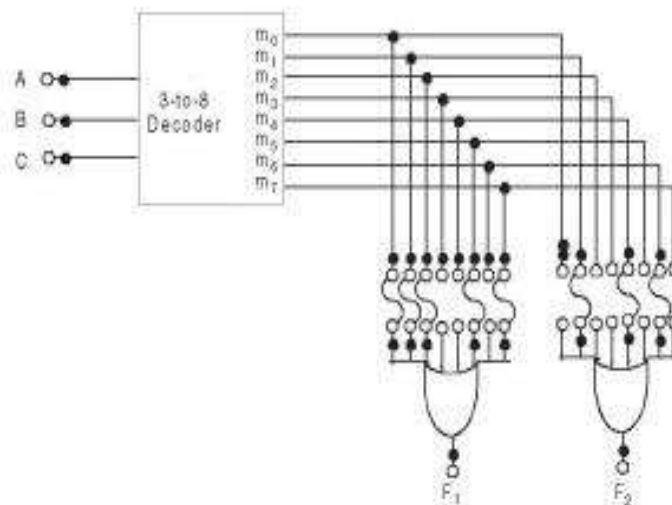

Example#2:

Design following equations on an 8x4 PROM

$$F_0 = (m_1 + m_5 + m_7)$$

$$F_1 = (m_1 + m_4)$$

$$F_2 = (m_0 + m_7)$$


$$F_3 = (m_2 + m_5 + m_7)$$

Digital Logic Design (ESC-151)

Abdul Rehman

email id:- abdul@northern.edu.pk

Whatsapp#03087792217

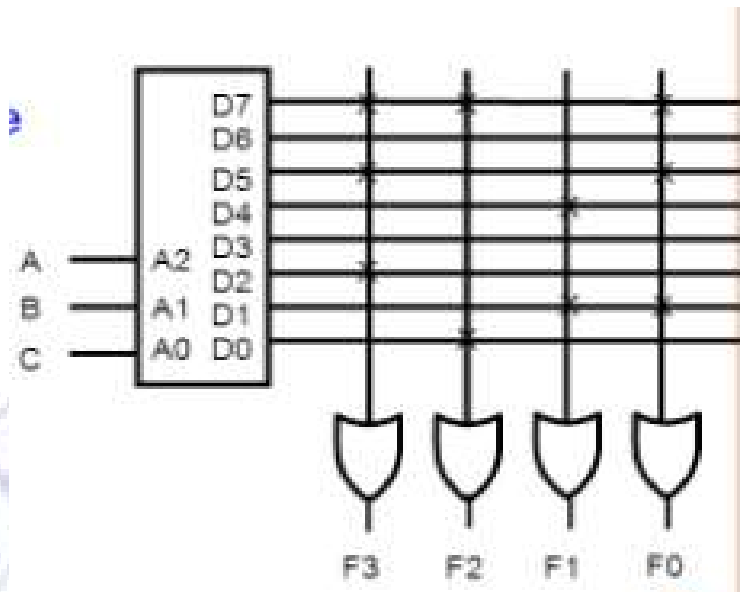

Example#3:

Implement following functions on an 8x3 PROM:

$$F1 = AB' + AC + B'$$

$$F2 = ABC + B'C + AC'$$

$$F3 = A'B'C' + A'B'$$

As, we are doing programming in PROM, where we use decoder for AND Array, and as you know that, in case of decoder, all the equations must be standard. So first convert these non-standard equations into standard equations and then we will be able to program these functions on a PROM.

$$F1 = AB' + AC + B'$$

AB'?	A?C	?B'?
1 00	1 01	000
1 01	111	001
		100
		101

$$F1 = ABC + A'B'C' + A'B'C + AB'C' + AB'C$$

$$F2 = ABC + B'C + AC'$$

Digital Logic Design (ESC-151)

Abdul Rehman

email id:- abdul@northern.edu.pk

Whatsapp#03087792217

ABC	?B'C	A?C'
111	001	100
	101	110

$$F2=ABC+A'B'C+AB'C+AB'C'+ABC'$$

$$F3= A'B'C'+A'B'$$

A'B'C'	A'B'?
000	000
	001

$$F3=A'B'C'+A'B'C$$

Resultant Standard Equations:

$$F1=ABC+A'B'C'+A'B'C+AB'C'+AB'C$$

$$F2=ABC+A'B'C+AB'C+AB'C'+ABC'$$


$$F3=A'B'C'+A'B'C$$

Digital Logic Design (ESC-151)

Abdul Rehman

email id:- abdul@northern.edu.pk

Whatsapp#03087792217

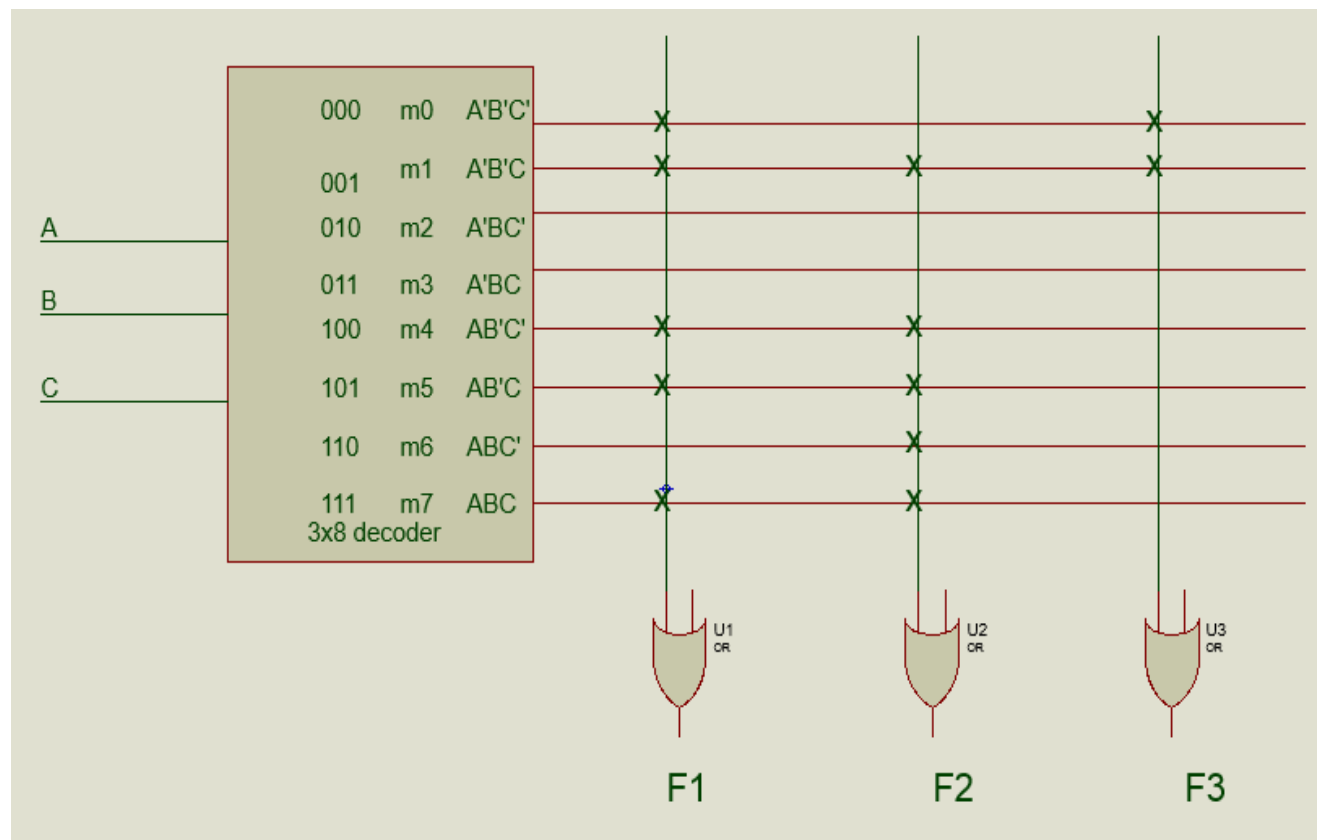


Practice Examples for Students:

Example#1:

Implement following functions on a 4x3 PROM:

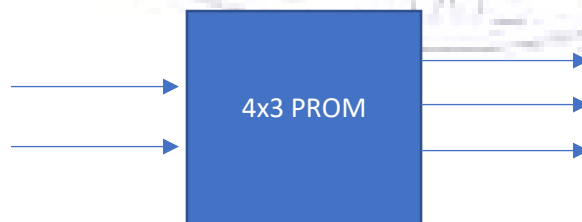1. $F1 = AB' + AB$
2. $F2 = AB + AB'$
3. $F3 = AB + A'B'$



Digital Logic Design (ESC-151)

Abdul Rehman

email id:- abdul@northern.edu.pk

Whatsapp#03087792217

Example#2:

Get equations from the given truth table and implement the output functions on a PROM. (Decide the order of PROM by your self)

<u>A</u>	<u>B</u>	<u>C</u>	<u>O1</u>	<u>O2</u>	<u>O3</u>
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	1	1	0
0	1	1	1	1	0
1	0	0	0	1	1
1	0	1	0	0	1
1	1	0	1	0	0
1	1	1	0	1	1

Example#3:

Design following equations on a PROM. (Decide the order of PROM first)

$$F1 = (A+B+C)(A'+B+C')(A'+B+C)$$

$$F2 = (A+B'+C')(A+B+C)(A'+B'+C')(A+B+C')$$

HINT: PROM makes use of decoder, and decoder's outputs are in SOP Form, so first convert the given POS Into SOP And then start designing

Assignment:11

Dear students read the given lectures carefully as per the course objectives mentioned on the top and carryout the assignment as per following instructions

Digital Logic Design (ESC-151)

Abdul Rehman

email id:- abdul@northern.edu.pk


Whatsapp#03087792217

Task to do:

1) Convert following equation into its equivalent NOR implementation:

$$(a+b+c') \text{ xor } (b.d)'$$

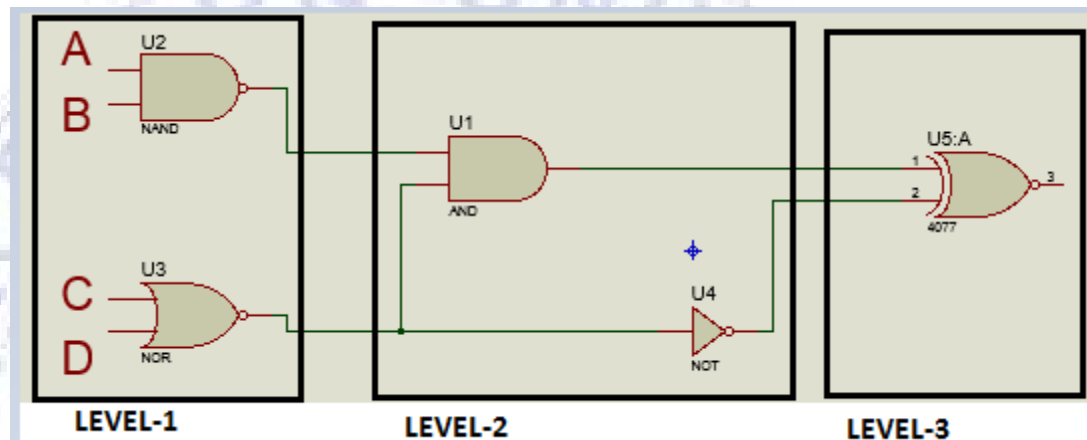2) Convert following circuit into equivalent NAND- NOR Implementation as per said in the given question:



- Level-1 into equivalent NAND implementation
- Level-2 into equivalent NOR implementation
- Level-3 into equivalent NAND implementation

Reference Material:

Lesson plans

Text book: Digital design by Moris Mano 4th edition

Also see digital fundamentals 8th ed by Floyd

Lecture Video Links:

part-1: <https://youtu.be/v-8ltNjOclM>

part-2: <https://youtu.be/H70LLK5SfDQ>

Digital Logic Design (ESC-151)

Abdul Rehman

email id:- abdul@northern.edu.pk

Whatsapp#03087792217

part-3: <https://youtu.be/nKK2X-akJuo>

part-4: <https://youtu.be/vBXRIAKrl9Q>

part-5: <https://youtu.be/asPZxhw7i8Q>

Lab Work: <https://youtu.be/4NIU6nSXCg8>

LAB Work:

Design the circuits given in this week assignment on proteus and send screenshots to Mr Hamza Sakhi via email at hamzasakhic97@gmail.com

Lab manuals have been uploaded on whatsapp and Edmodo library section.

