

Objectives:


The objective for this week will be to do detailed discussion on combinational circuit designing with practice examples:

- 1x4 De- Multiplexer
- 1x8 De-Multiplexer
- Don't care conditions at input side of truth table
- Water level Indicator
- Don't care conditions at output side of truth table
- Elevator control system

LECTURE-19

DESIGN A 1x4 DE-MULTIPLEXER

Block diagram:

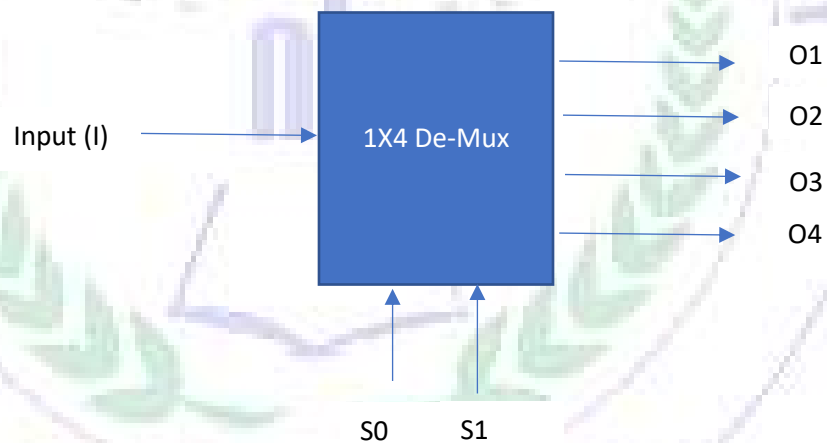

Truth Table:

Digital Logic Design (ESC-151)

Abdul Rehman

email id:- abdul@northern.edu.pk

Whatsapp#03087792217

<u>S₀</u>	<u>S₁</u>	<u>I</u>	<u>O1</u>	<u>O2</u>	<u>O3</u>	<u>O4</u>
0	0	0	0	0	0	0
0	0	1	1	0	0	0
0	1	0	0	0	0	0
0	1	1	0	1	0	0
1	0	0	0	0	0	0
1	0	1	0	0	1	0
1	1	0	0	0	0	0
1	1	1	0	0	0	1

Output Equations:

$$\underline{O1} = S_0' S_1' I$$

$$\underline{O2} = S_0' S_1 I$$

$$\underline{O3} = S_0 S_1' I$$

$$\underline{O4} = S_0 S_1 I$$


Circuit Diagram:

Digital Logic Design (ESC-151)

Abdul Rehman

email id:- abdul@northern.edu.pk

Whatsapp#03087792217

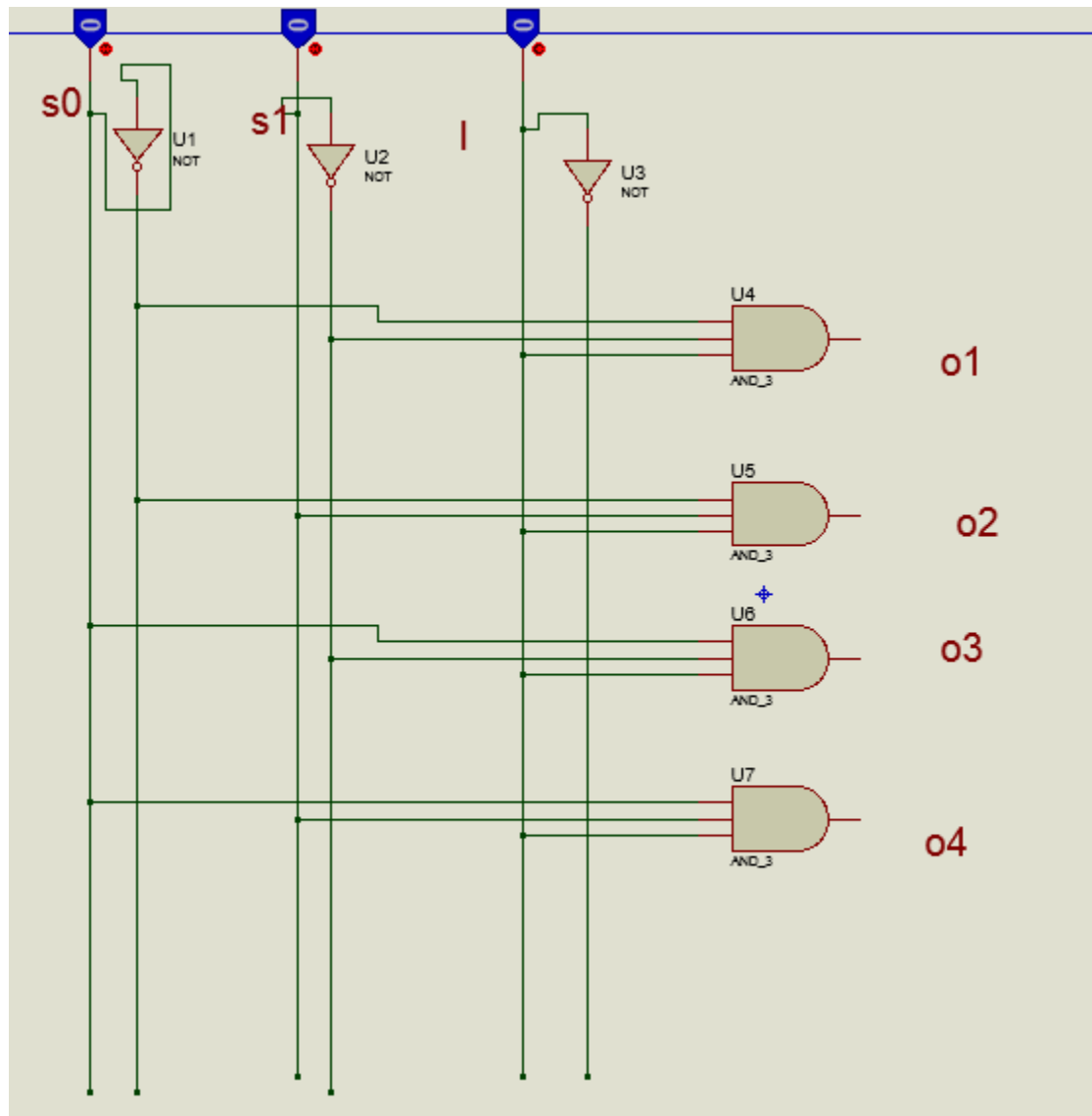

Digital Logic Design (ESC-151)


Abdul Rehman

email id:- abdul@northern.edu.pk

Whatsapp#03087792217

DESIGN A 1x8 DE-MULTIPLEXER

Block Diagram:

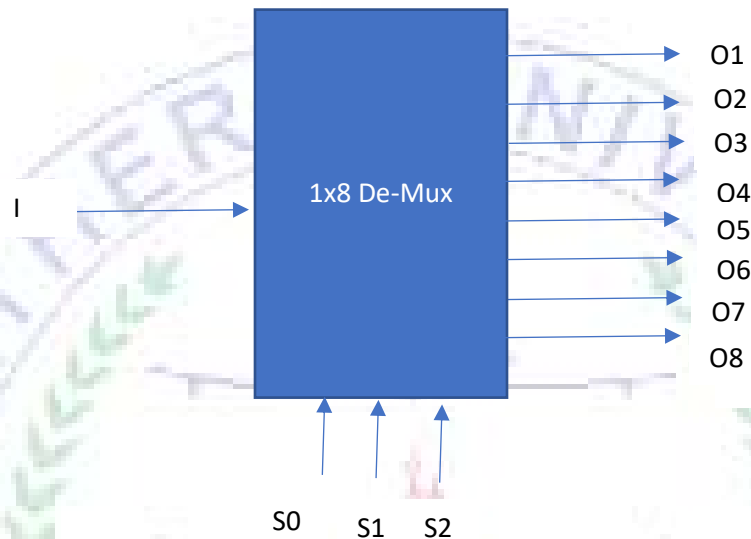

Truth Table:

<u>S0</u>	<u>S1</u>	<u>S2</u>	<u>outputs</u>	
0	0	0	I=O1	$O1 = S_0' S_1' S_2' I$
0	0	1	I=O2	$O2 = S_0' S_1' S_2 I$
0	1	0	I=O3	$O3 = S_0' S_1 S_2' I$
0	1	1	I=O4	$O4 = S_0' S_1 S_2 I$
1	0	0	I=O5	$O5 = S_0 S_1' S_2' I$
1	0	1	I=O6	$O6 = S_0 S_1' S_2 I$
1	1	0	I=O7	$O7 = S_0 S_1 S_2' I$
1	1	1	I=O8	$O8 = S_0 S_1 S_2 I$

Output Equations:

$$O1 = S_0' S_1' S_2' I$$

$$O2 = S_0' S_1' S_2 I$$

Digital Logic Design (ESC-151)

Abdul Rehman

email id:- abdul@northern.edu.pk

Whatsapp#03087792217

$$O3 = s_0' s_1 s_2' I$$

$$O4 = s_0' s_1 s_2 I$$


$$O5 = s_0 s_1' s_2' I$$

$$O6 = s_0 s_1' s_2 I$$

$$O7 = s_0 s_1 s_2' I$$

$$O8 = s_0 s_1 s_2 I$$

Circuit Diagram:

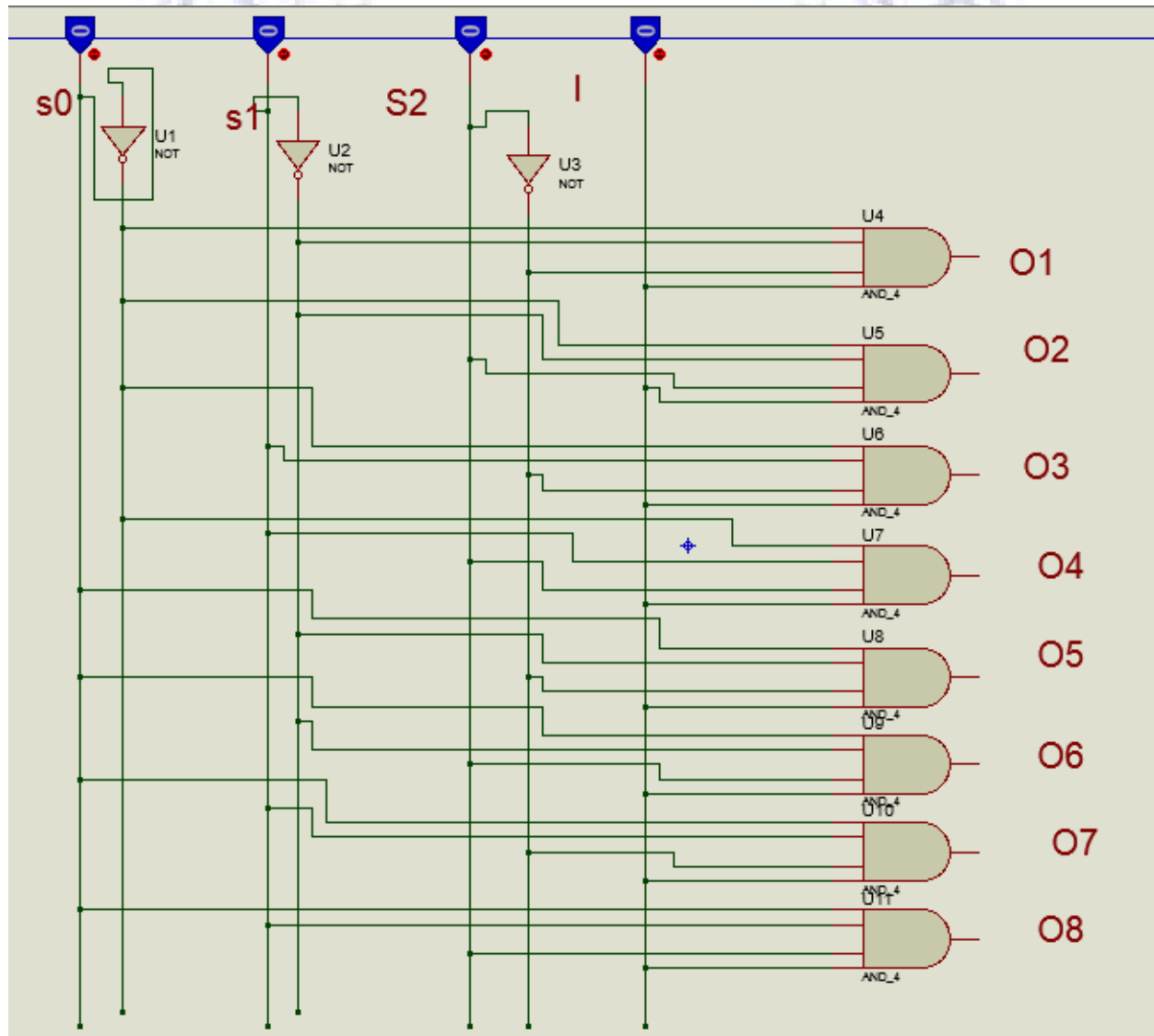

Digital Logic Design (ESC-151)

Abdul Rehman

email id:- abdul@northern.edu.pk

Whatsapp#03087792217

DON'T CARE CONDITIONS AT INPUT SIDE (PRACTICE EXAMPLES)

EXAMPLE#1

<u>A</u>	<u>B</u>	<u>C</u>	<u>OUTPUT</u>
0	0	0	1
X	1	1	1
0	x	1	1
1	x	x	1

000	X11	0x1	1xx
	011	001	100
	111	011	101
			110
			111

BC	00	01	11	10
A	1	1	1	
0	1	1	1	
1	1	1	1	1

$$\text{OUTPUT} = A + B' + C$$

EXAMPLE#2

<u>A</u>	<u>B</u>	<u>C</u>	<u>OUTPUT</u>
0	1	X	1
1	X	0	1
1	1	X	1
X	0	X	1
0	0	0	1

01X | 1X0 | 11X | X0X | 000

Digital Logic Design (ESC-151)

Abdul Rehman

email id:- abdul@northern.edu.pk

Whatsapp#03087792217

010	100	110	000	
011	110	111	001	
			100	
			101	

BC A	00	01	11	10
0	1	1	1	1
1	1	1	1	1

OUTPUT=1

EXAMPLE#3

<u>A</u>	<u>B</u>	<u>C</u>	<u>D</u>	<u>OUTPUT</u>
0	X	X	0	1
X	1	1	1	1
X	1	X	0	1
0	X	1	1	1
1	1	X	1	1

0XX0	X111	X1X0	0X11	11X1
0000	0111	0100	0011	1101
0010	1111	0110	0111	1111
0100		1100		
0110		1110		

Digital Logic Design (ESC-151)

Abdul Rehman

email id:- abdul@northern.edu.pk

Whatsapp#03087792217


CD	00	01	11	10
AB				
00	1		1	1
01	1		1	1
11	1	1	1	1
10				

$$\text{OUTPUT} = AB + A'D' + A'C$$

LECTURE-20

DESIGN A BASIC WATER LEVEL INDICATOR

Block diagram:

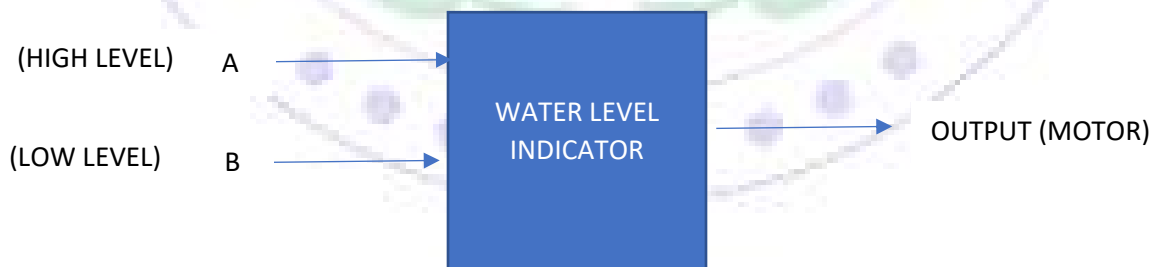

Truth Table:

Digital Logic Design (ESC-151)

Abdul Rehman

email id:- abdul@northern.edu.pk

Whatsapp#03087792217

A	B	OUTPUT
0	0	0
0	1	1
1	0	0
1	1	X


Output Equations:

B	0	1
A		
0		1
1		X

Output Equation:

OUTPUT (motor)= B

Circuit Diagram:

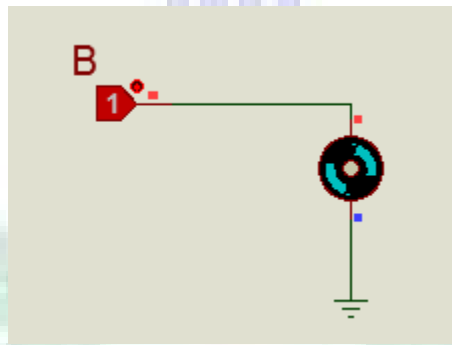

LETS DO SOME PRACTICE OF DON'T CARE CONDITIONS AT OUTPUT:

EXAMPLE#1

A	B	C	OUTPUT
0	0	0	0

Digital Logic Design (ESC-151)

Abdul Rehman

email id:- abdul@northern.edu.pk

Whatsapp#03087792217

0	0	1	1
0	1	0	X
0	1	1	X
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	X

BC \ A	00	01	11	10
0		1	X	X
1	1	1	X	

OUTPUT = $AB' + C$

EXAMPLE#2

A	B	C	OUTPUT
0	0	0	1
0	0	1	X
0	1	0	X
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

BC \ A	00	01	11	10
0	1	X	1	X
1			1	

OUTPUT = $A' + BC$

EXAMPLE#3

Digital Logic Design (ESC-151)

Abdul Rehman

email id:- abdul@northern.edu.pk

Whatsapp#03087792217


<u>A</u>	<u>B</u>	<u>C</u>	<u>D</u>	<u>OUTPUT</u>
0	0	0	0	1
0	0	0	1	0
0	0	1	0	X
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	X
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	X
1	1	1	0	0
1	1	1	1	0

CD	00	01	11	10
AB				
00	1		1	X
01	1		X	
11	1	X		
10	1	1		

OUTPUT= $C'D' + AC' + A'CD$

DESIGN A BASIC ELEVATOR CONTROL SYSTEM

Block diagram:

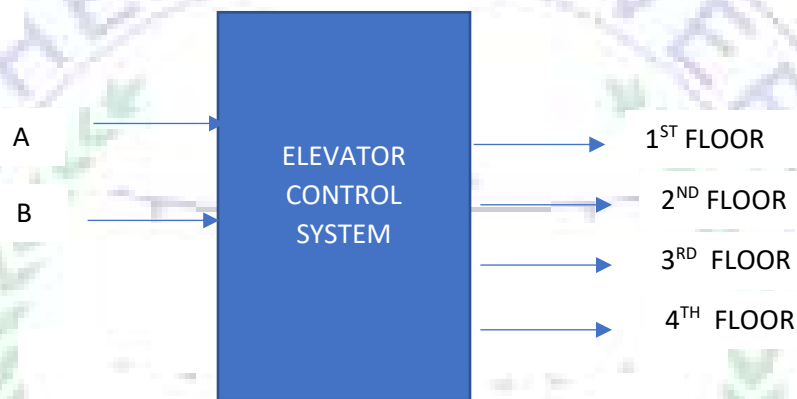

Truth Table:

<u>A</u>	<u>B</u>	<u>1ST</u> <u>FLOOR</u>	<u>2ND</u> <u>FLOOR</u>	<u>3RD</u> <u>FLOOR</u>	<u>4TH</u> <u>FLOOR</u>
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

Output Equations:

1st FLOOR= $A'B'$

2ND FLOOR= $A'B$

3RD FLOOR= AB'

4TH FLOOR= AB


Digital Logic Design (ESC-151)

Abdul Rehman

email id:- abdul@northern.edu.pk

Whatsapp#03087792217

Circuit Diagram:

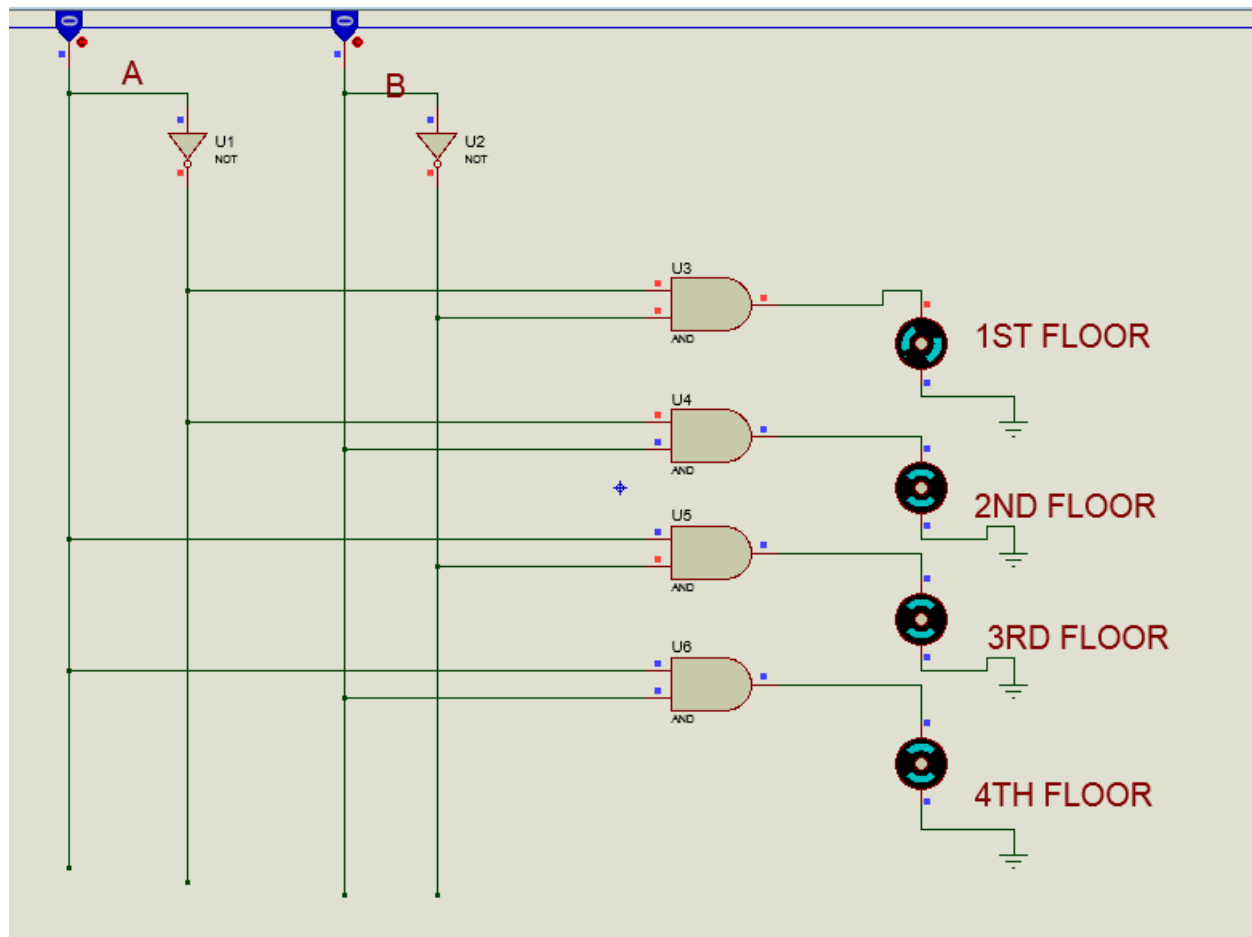

Digital Logic Design (ESC-151)

Abdul Rehman

email id:- abdul@northern.edu.pk

Whatsapp#03087792217

Assignment:10

Dear students read the given lectures carefully as per the course objectives mentioned on the top and carryout the assignment as per following instructions

Task to do:

Draw 10 random truth tables with 3,4 and 5 variables for your self, place don't care at inputs and outputs 5 each. Solve them and submit your assignment

Reference Material:

Lesson plans

Text book: Digital design by Moris Mano 4th edition

Also see digital fundamentals 8th ed by Floyd

Lecture Video Links:

Part-1: <https://youtu.be/jztGSeYMb28>

Part-2: <https://youtu.be/2cd6jiDI-xc>

Part-3: <https://youtu.be/urfQxDR7i6o>

Part-4: <https://youtu.be/TPe8JcbQzEQ>

Lab Work: <https://youtu.be/F0fn2OKpxdA>

LAB Work:

Design any 3circuits of given assignments on proteus and send screenshots to Mr Hamza Sakhi via email at hamzasakhic97@gmail.com

Digital Logic Design (ESC-151)

Abdul Rehman

email id:- abdul@northern.edu.pk

Whatsapp#03087792217

Lab manuals have been uploaded on whatsapp and Edmodo library section.

